

VLSI Design Practical 5 ExOR and ExNOR.


Ex OR dsch.

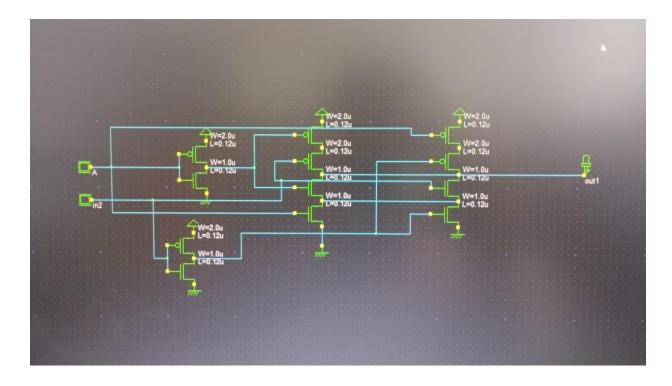


Waveform dsch.

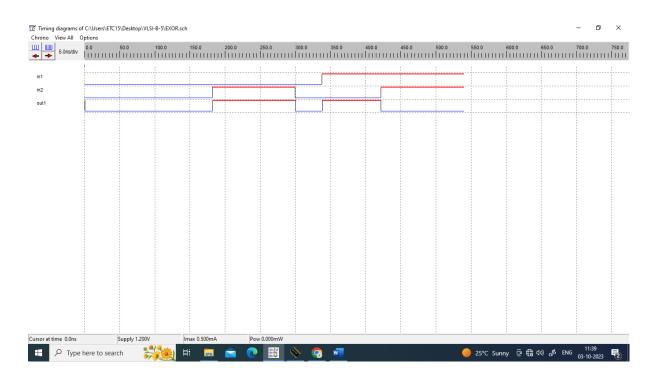


Ex OR Microwind.

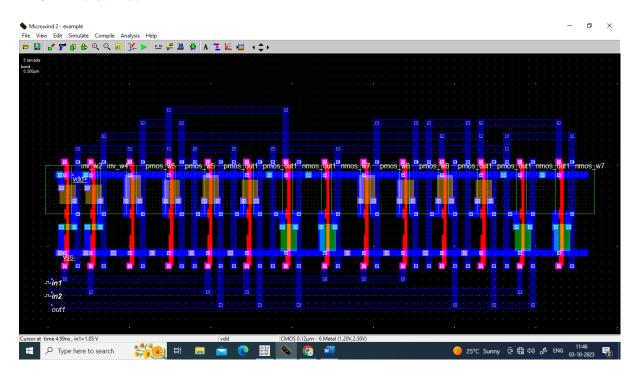


Waveform Microwind.

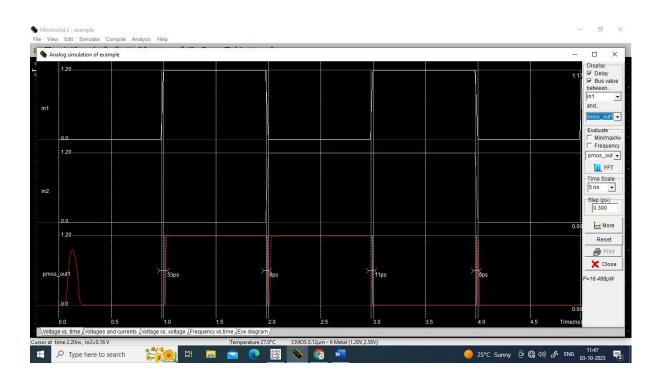


Ex NOR dsch.

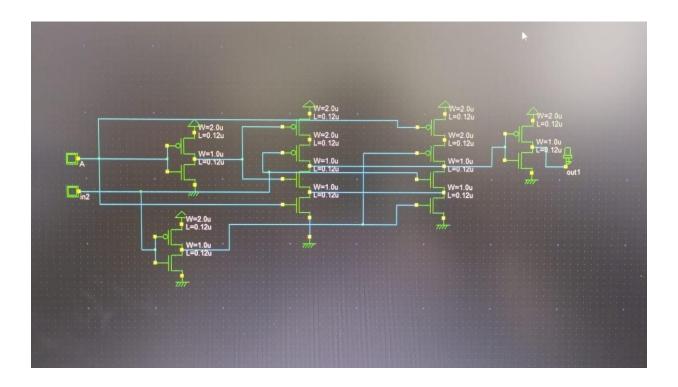

Waveform dsch.

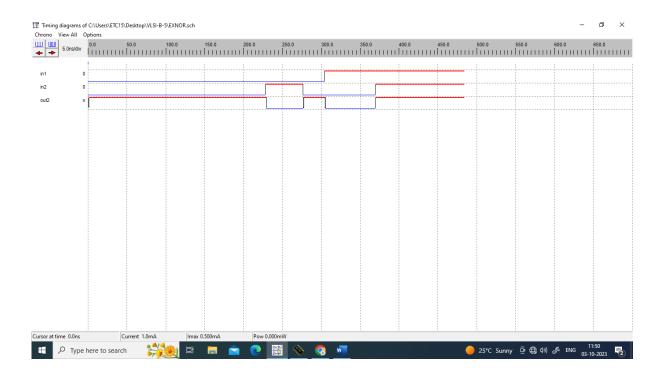

Ex NOR Microwind.

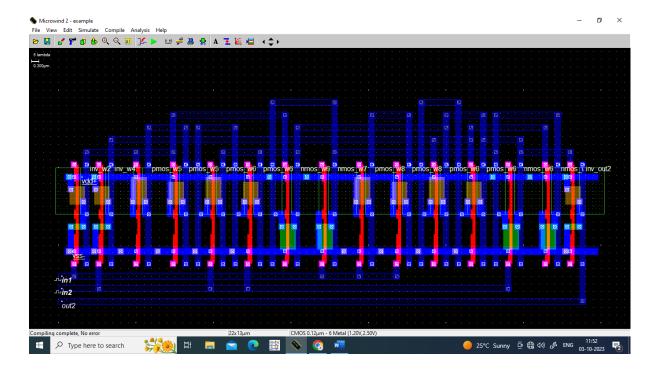

Waveform Microwind.

